

國立臺灣海洋大學 101 學年度研究所碩士班暨碩士在職專班入學考試試題

考試科目：電子學

系所名稱：光電科學研究所碩士班不分組

\* 可使用計算器

1. 答案以橫式由左至右書寫。2. 請依題號順序作答。

1. A uniform bar of n-type silicon of  $5\ \mu\text{m}$  length has a voltage of 1 V applied across it. If the dopant concentration  $N_D=10^{17}\ \text{cm}^{-3}$  and the electron mobility  $\mu_n=1350\ \text{cm}^2\text{V}^{-1}\text{s}^{-1}$ , find (a) the electron drift velocity, (b) the time it takes an electron to cross the  $5\text{-}\mu\text{m}$  length, (c) the drift-current density, and (d) the drift current in the case the silicon bar has a cross sectional area of  $0.36\ \mu\text{m}^2$ . (17%)
2. Assuming that the diodes in the circuits of Fig. 1 are ideal, find the values of the labeled currents and voltages. (11%)
3. For the circuit in Fig. 2, it is required to determine the value of the voltage  $V_{BB}$  that results in the transistor operating (a) in the active mode with  $V_{CE}=4\ \text{V}$ , (b) at the edge of saturation, (c) deep in saturation with  $\beta_{\text{forced}}=10$ . Assume that  $V_{BE}$  remains constant at 0.7 V and the transistor at the edge of saturation has  $V_{CE\text{sat}}=0.3\ \text{V}$ , while the transistor deep in saturation has  $V_{CE\text{sat}}=0.2\ \text{V}$ . The transistor  $\beta$  is specified to be 60. (17%)
4. The NMOS transistors in the circuit of Fig. 3 have the threshold voltage  $V_t=0.5\ \text{V}$ , the process transconductance parameter  $\mu_n C_{\text{ox}}=125\ \mu\text{AV}^{-2}$ , and channel length  $L_1=L_2=1\ \mu\text{m}$ . Find the required values of gate width for each of  $Q_1$  and  $Q_2$ , and the value of  $R$ , to obtain the voltage and current values indicated. Neglect the channel length modulation effect ( $\lambda=0$ ). (9%)
5. The noninverting op-amp configuration shown in Fig. 4. (a) Assume that the op amp has infinite input resistance and zero output resistance. Find an expression for the feedback factor  $\beta$ . (b) If the open-loop gain  $A=10^3\ \text{V/V}$ , find  $R_2/R_1$  to obtain a closed-loop gain  $A_f$  of 10 V/V. (c) If  $A$  decrease by 30%, what is the corresponding decrease in  $A_f$ ? (11%)
6. For the circuit of Fig. 5 with  $V=12\ \text{V}$ ,  $R_1=20\ \text{k}\Omega$ ,  $R_f=60\ \text{k}\Omega$ ,  $R_2=R_5=10\ \text{k}\Omega$ , and  $R_3=R_4=4\ \text{k}\Omega$ , find the limiting levels and the value of  $v_I$  at which the limiting levels are reached. Also determine the limiter gain and the slope of the transfer characteristic in the positive and negative limiting regions. Assume that diode voltage  $V_D=0.7\ \text{V}$ . (20%)
7. For the CMOS class AB output stage of Fig. 6, consider the case of matched  $Q_1$  and  $Q_2$ , and matched  $Q_N$  and  $Q_P$ . If quiescent current  $I_Q=1.2\ \text{mA}$  in  $Q_N$  and  $Q_P$ , find  $(W/L)$  for each of  $Q_1$ ,  $Q_2$ ,  $Q_N$ , and  $Q_P$  so that in the quiescent state each transistor operates at an overdrive voltage of 0.2 V. Let  $V_{DD}=V_{SS}=2.5\ \text{V}$ , the process transconductance parameter  $k'_n=200\ \mu\text{AV}^{-2}$ ,  $k'_p=100\ \mu\text{AV}^{-2}$ , and the threshold voltage  $V_{tn}=-V_{tp}=0.6\ \text{V}$ . Also find  $V_{GG}$ . Assume that  $I_{\text{BIAS}}=0.3\ \text{mA}$  and neglect the channel length modulation effect ( $\lambda=0$ ). (15%)

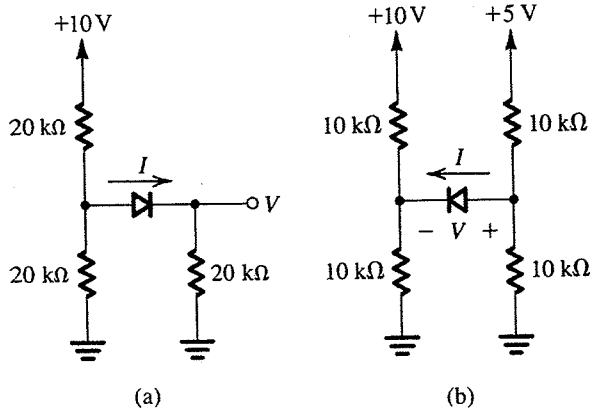


Fig. 1

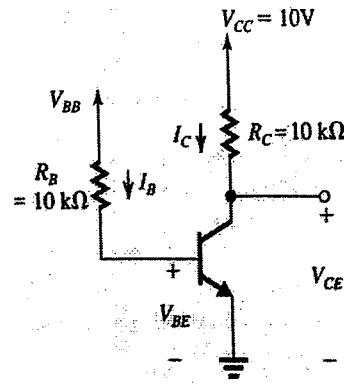


Fig. 2

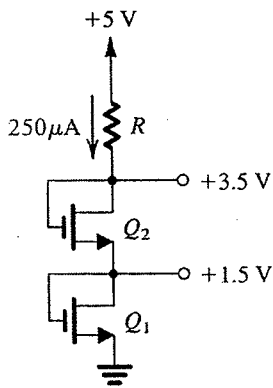


Fig. 3

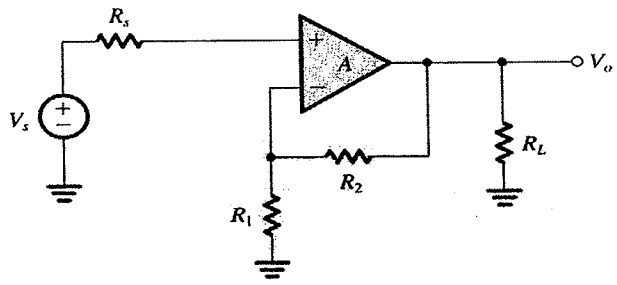


Fig. 4

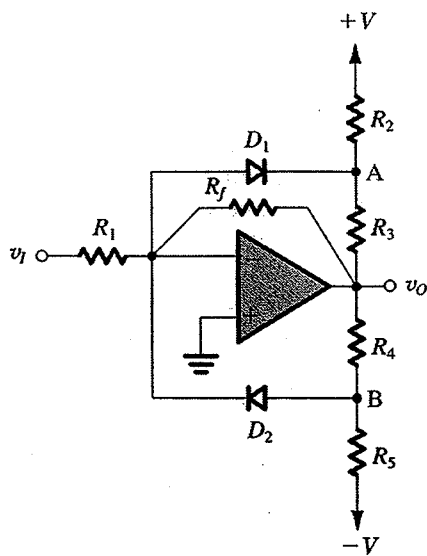


Fig. 5

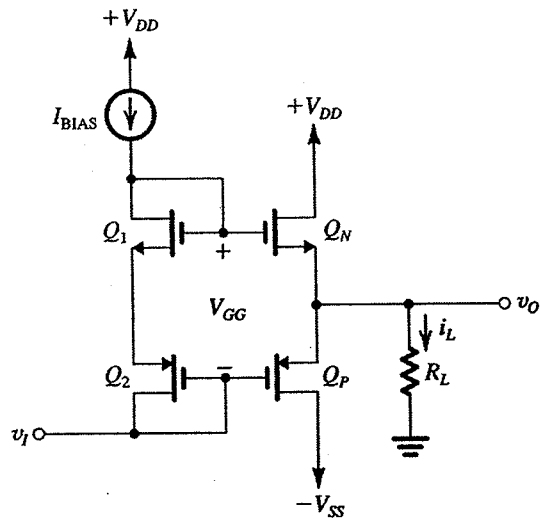


Fig. 6