

國立臺灣海洋大學一〇二學年度研究所碩士班暨碩士在職專班招生考試試題

考試科目： 電子學（含半導體元件物理）

系所名稱： 電機工程學系碩士班固態電子組

※可使用計算器

1.答案以橫式由左至右書寫。2.請依題號順序作答。

註 1：請配合將各大題作答在同一區塊並標明題號(如 1(a)、3(b)...)。

註 2：重要參數或計算值請參酌


註 2：可使用計算機

1、Give a resistor-diode circuit with I-V characteristics of the diode shown as follows. Where C is large enough for small signal  $v_s$ .  $V_D(I_D)$  and  $v_d(i_d)$  are from  $V_S$  and  $v_s$ , respectively.

(a) If  $V_S=3$  volt,  $v_s=0$ , and  $R=240\Omega$ , find the current flowing through the diode. 2%

(b) If  $V_S=3$  volt,  $v_s=2\sin(\omega t)$  milli-volt and  $R=240\Omega$ , find the current flowing through the diode. 3%

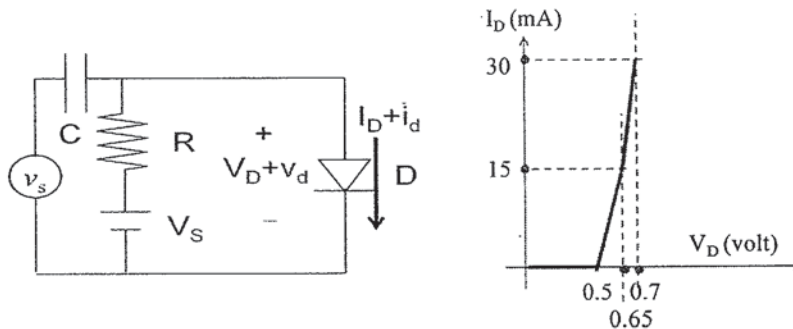(c) If  $V_S=5$  volt,  $v_s=2\sin(\omega t)$  milli-volt and  $R=200\Omega$ , find the current flowing through the diode. 5%



2、For a Si p-n junction diode with the p- and n-side doped with  $10^{16}$  B atom/cm<sup>3</sup> and  $2 \times 10^{16}$  As atom/cm<sup>3</sup>, respectively. When the diode is reverse-biased by a voltage of  $V_R$ , the depletion width found on the n-side is 0.5 micron. Then

(a) Determine the built-in voltage associated with the diode at equilibrium. (Intrinsic concentration  $n_i=10^{10}$  /cm<sup>3</sup>) 2%

(b) Determine the depletion width on the p-side of the diode at  $V_R$  (F/cm<sup>2</sup>). 2%

(c) Find the depletion capacitance  $C_T$  of the diode at  $V_R$ . 2%

(d) Calculate the bias voltage  $V_R$ . 2%

3、A voltage amplifier is shown as follows. For the bipolar transistor, the on-voltage of emitter-base junction is fixed at 0.7 volt and the saturation voltage between the emitter and collector is  $\approx 0.2$  volt. Knowing that  $V_{EE}=1.7$  volt,  $V_{CC}=6$  volt, and  $R_E=0.5$  k $\Omega$ .


(a) What kind of the transistor, n-p-n or p-n-p? 2%%

(b) If the common emitter current gain  $\beta_F=99$ , determine the common-base current gain  $\alpha_F$ . 2%

(c) With a known  $\alpha_F=0.95$ , determine  $V_C$  and  $I_C$  for  $R_C=2$  k $\Omega$  and  $v_s=0$  volt. 3%

(d) Along with problem (c), if  $v_s=2.5\cos(\omega t)$  milli-volt find the  $v_o=?$ 3%

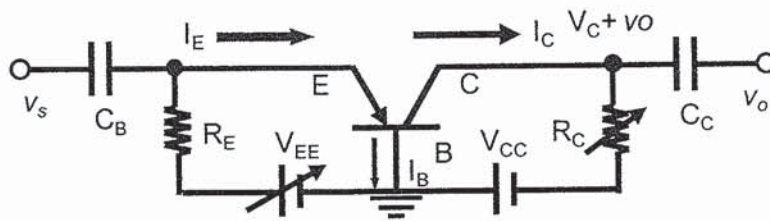
(e) Assuming the base transport factor is idealized ( $\alpha_T \approx 1$ ) with an emitter injection efficiency of  $\gamma=0.98$ , determine the voltage gain  $A_v$ , input and output resistance ( $R_i$  and  $R_o$ ) for  $R_C=2$  k $\Omega$ . 5%




4 · For an Al-SiO<sub>2</sub>-Si MOS diode shown as follows on the left hand side, the voltage across the Si-substrate occurring strong inversion is  $V_{Sub} \approx 0.7$  volt.

- Find the maximum depletion width,  $W_{max}$ , of the Si-substrate. [See hint] 2%
- For a  $d=14$  nm, calculate the value of the capacitor,  $C_{ox}$  (F/cm<sup>2</sup>). 2%
- Along with problems (a) and (b), determine the threshold voltage  $V_T$  that results in strong inversion. 2%
- If  $V_T=5$  V is required, find the new value of oxide thickness  $d'$ . 4%
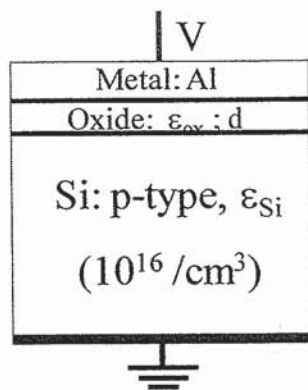
$$Hint : V_{Sub} = \frac{qN_A W^2}{2\epsilon_{Si}}$$


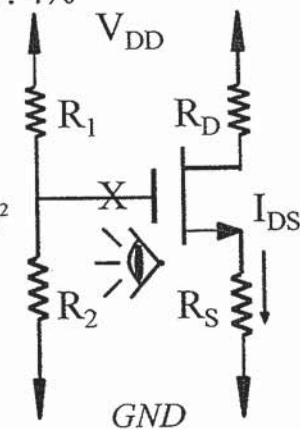
$$I_{DS} = k_n \frac{W}{L} (V_{GS} - V_T)^2$$




5 · Enhancement-mode MOSFET circuits biased as a discrete-component amplifier is shown above on the right hand side with saturation current expression. Where  $k_n=50 \mu A \cdot V^{-2}$ ,  $W/L=10$ , and  $V_T=1$  volt,  $V_{DD}=6$  volt,  $R_1=R_2=1$  M $\Omega$ ,  $R_D=2R_S=4$  k $\Omega$ .

- Find the Thevenin's equivalent circuit left seeing from marker "X",  $V_{th}$  and  $R_{th}$ . 4%
- Using the result in (a) to determine  $I_{DS}$  and  $V_{DS}$ . 4%
- Calculate the transconductance  $g_m$  used in small-signal models. 2%

6 · An op-amp circuit shown as follows (left circuit). The power supply used in op-amp IC is  $\pm 15$  volt.

- Find  $V_3$ ,  $V_4$ , and  $V_5$  for  $V_1=V_2=2$  volt. 5%
- Find  $V_3$ ,  $V_4$ , and  $V_5$  for  $V_1=1.5$  V,  $V_2=1$  V. 5%

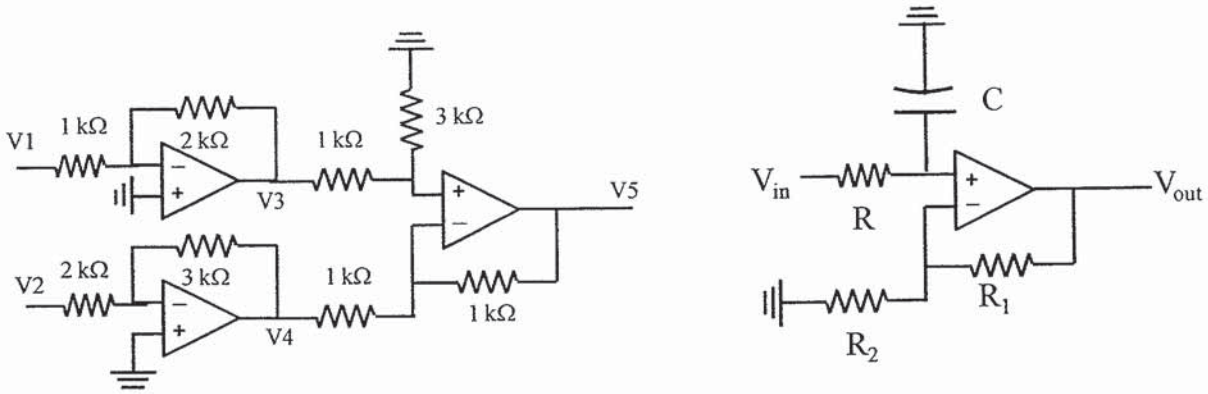
7 · Circuit shown as follows on the right hand side is a single-pole filter. Please determine the critical frequency and closed-loop voltage gain in the pass band. Where  $R=0.5$  k $\Omega$ ,  $R_1=10$  k $\Omega$ ,  $R_2=2$  k $\Omega$ , and  $C=40$  nF. 6%



8 · Sketch the CMOS inverter and explain briefly its operation. 10%

9 · A BJT amplifier is shown as follows with  $\beta_f=120$  and an on-voltage of **0.8 volt** for the E-B junction.  $V_{CC}=12$  volt,  $R_1=800$  k $\Omega$ ,  $R_2=200$  k $\Omega$ ,  $R_C=5$  k $\Omega$ ,  $R_L=10$  k $\Omega$ ,  $C_B=0.2$   $\mu$ F and  $C_C=0.3$   $\mu$ F.

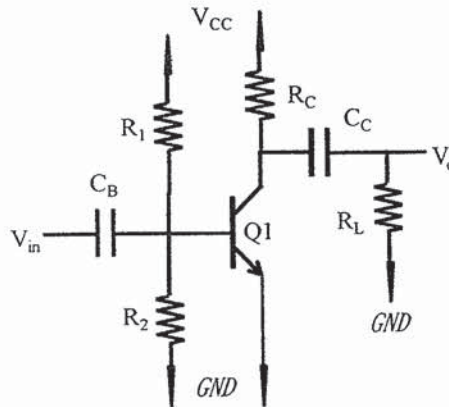- (a) Determine bias current  $I_C$  and  $V_{CE}$ . 5%
- (b) Find the voltage gain in mid-frequency range. 5%
- (c) Determine the total low-frequency response. 5%



10 · For a full-wave bridge rectifier with idealized diodes, the input signal is  $v_s=5\sin(2\times 10^3t)$  volt.

- (a) Determine the frequency of the output signal. 2%
- (b) Calculate the equivalent direct voltage,  $V_{dc}$ , and  $V_{rms}$  value. 4%

$$V_T = \frac{kT}{q} \approx 25mV \quad \epsilon_{Si} \approx 10^{-12} F/cm \quad \epsilon_{ox} \approx 3.5 \times 10^{-13} F/cm$$

x	1	2	3	5	7
e <sup>x</sup>	2.72	7.39	20.08	148.41	1096.6
ln(x)	0	0.693	1.099	1.609	1.946